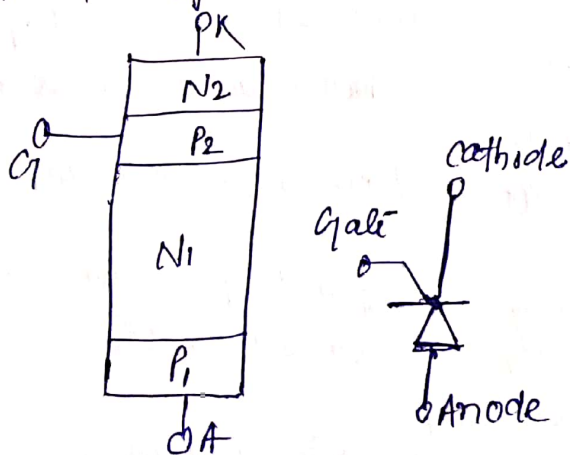


CHAPTER - 2 Thyristor Valves

- HVDC converters are combination of valves which have the property of conducting in the forward direction and blocking in the reverse direction.
- The term "valve", carried over from mercury arc valve, is applied now for thyristor valves which are made up of series and parallel connection of many thyristor cell or devices.
- Thyristor valves are used in line commutated converters, IGBT valves are used in voltage source converters.
- The major problem with the mercury valves is occurrence of arc backs (back fires) which result in the destruction of the rectifying property of the valves.
- Arc backs are random phenomena, result in failure to block in reverse direction.
- Arc backs can be reduced by carefully that to be partially, arc backs are non-self-clearing and result in line to line faults which stress transformer windings and anodes in the valves.
- Thyristor valves were developed in late sixties have eliminated all these problems.

Thyristor device :-

- Thyristor is defined as a range of four layer (PNPN) semiconductor switches. It is also known as silicon controlled rectifier (SCR).
- The structure of a thyristor with the gate terminals and its electrical symbol are shown in below figure.



Layer structure and symbol of a thyristor.

- The device is uni (one) direction from anode to cathode and conduction can be controlled by the gate.
- Avoids the necessity of 11k connections, the voltage rating is insufficient to make up a high voltage valve. Thus, a series connection is introduced and it have some problems which are considerable.
- increasing the voltage rating of a thyristor is easy, but it is at cost of increased losses, turn-off times and reduced peak allowable junction temp.s.
- The capacity of a thyristor to stand high voltages depends on the d. material of a device is made up.

Device characteristics :-

→ The device have following 3 states :-

- Forward biased and blocking
- Forward biased and conducting
- Reverse biased and blocking.

→ The second state is called turn-on, and the third state is called turn off.

Steady state characteristics :-

Off-state :- The volt-ampere characteristics of the device are shown in below figure.


- During the off state (both forward and reverse blocking), only a small magnitude of leakage current flows (100mA).
- The blocking capability with gate open is specified in terms of limiting repetitive peak forward (V_{DRM}) or reverse (V_{RRM}) voltages.


→ A non repetitive peak reverse voltage rating (V_{RRM}) is specified and rated junction temp of the thyristor (typically $125^{\circ}C$)

→ Variation of V_{RRM} voltage ratings with J_{unc} temp. is as shown in fig. below. for different levels of rated reverse current.

Here $M = \text{Max } J_{unc}$ rated J_{unc} temp.

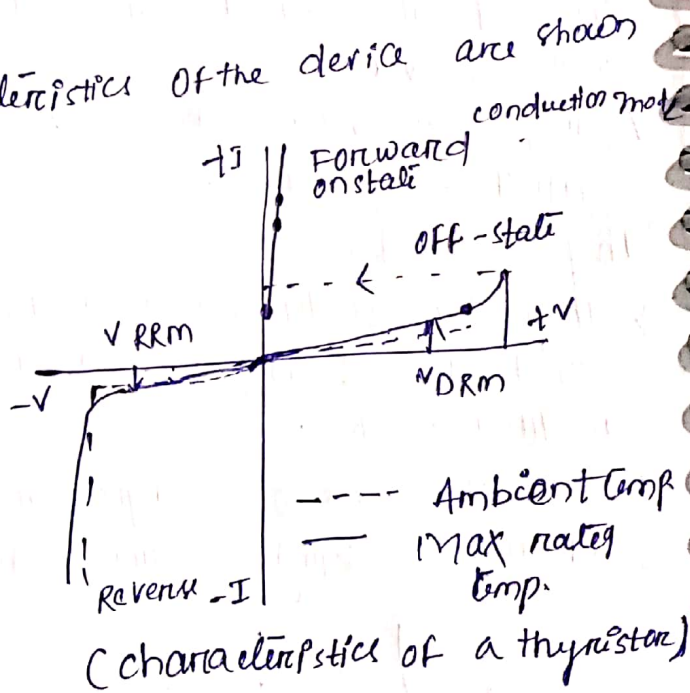→ Effect of increasing the reverse current is to increasing the ratings.



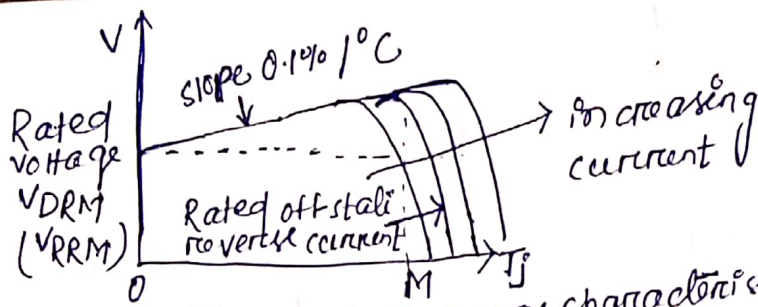

V_{DRM} = Repetitive Peak Forward Voltage
 V_{RRM} = Repetitive Peak Reverse Voltage

(Fig. Typical thyristor off-state voltage characteristics as a function of junction temp.)
 → The behaviour of thyristors under transient voltages is not well understood. However, according to one particular study, the following conclusions can be drawn.

1. The transient breakover voltage of a thyristor is independent of its voltage ratings.
2. The forward breakover voltage of a thyristor under a transient voltage may be lower than its voltage rating and decreases with increase in junction temp.
3. The instant of forward break over of a thyristor can frequently occur on the tail of the applied voltage wave. This is due to minimum charge and time delay of the thyristor.
4. The reverse breakover voltage levels of a thyristor under slow transients (30/600 μ s) can be lower compared to fast (1.2/50 μ s).

→ Reverse direction of thyristor can cause energy losses which is cause variation of the reverse avalanche current with the voltage magnitude of the reverse voltage.

→ The transient voltage blocking of a thyristor is related to the critical power to damage the device.

→ Cumulative effects due to transients with less than critical power cause degradation of the device.


On-Static :-

→ There are a number of electrical and thermal parameters that characterize the on-state behaviour. Some of these are as follows.

1. On-state voltage (V_M)
2. Mean (average) on-state current (I_{TAV})
3. Root mean square value of the on-state current (I_{TRMS})
4. Surge (non-repetitive) on-state current (I_{TSM})
5. Non-repetitive survival rating ($I^2 t$)

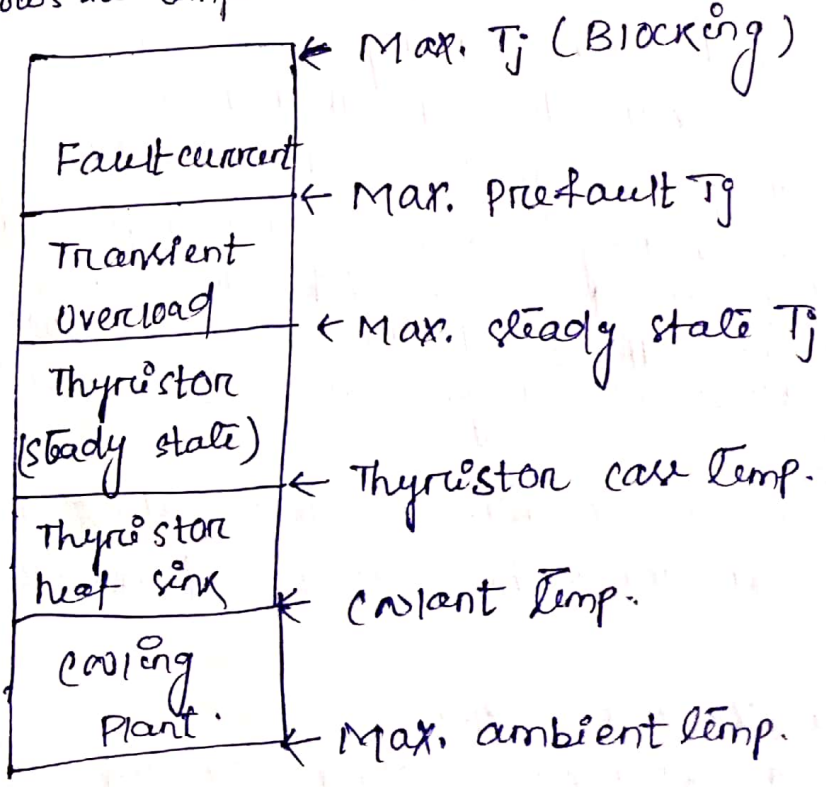- 6. Holding current (I_H)
- 7. operating temperature range
- 8. Junction to case thermal resistance (R_{thjc})
- 9. contact thermal resistance.

- Thyristor on state, in forward conducting state, voltage is anode to cathode and also it having forward voltage drop.
- it is an important to affecting the power losses during on-state & the off operation of thyristor.
- on-state voltage depends on a number of factors.
- The power losses at current density around $100A/cm^2$ is due to recombinations.
- The power losses at current density around $1000A/cm^2$ is due to ohmic heating.
- silicon wafers of small thickness and long carrier life time give low on-state voltages, so increasing the carrier life time also increase turn off time. if optimize both may result the reverse recovery current.
- current ratings of on-state is determined by the junction temperature. it must be kept below the value necessary to ensure that can be block recovery voltage after a worst case credible over current.
- Fig. below shows the temp. build up in a thyristor valve.




where $T_j =$
 junction temp. of a
 thyristor.

(Fig. Temp. build up in a thyristor)


- The surge current capability of a thyristor is based on its filamentation temp.
- The requirement to have surge suppression capability result in operation of the thyristor at reduced j_{avg} temp.
- The max^m j_{avg} temp. attained due to the cumulative effects caused by passage of repeated current surges should be below thyristor filamentation temp.
- Holding current (I_H), is required ~~min~~ minimum current to maintain thyristor on-state.
- Forward current reduced, the turn-off occurs when recombination occurs.
- The I_H reduces with $\uparrow j_{avg}$ temp.

Switching characteristics :-

Turn-on :-

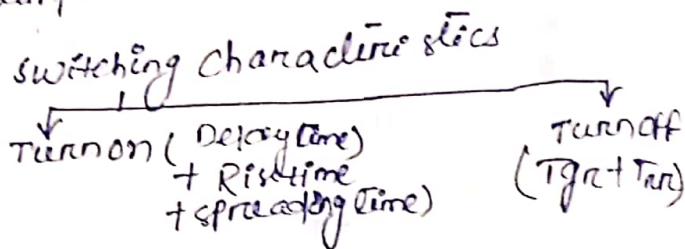

- A gate drive is applied with the forward voltage above latching voltage, turn-on occurs.
- Because of finite sheet resistance of the P-base region, only regions of the cathode nearest to the gate are influenced by gate current.
- ~~Regenerat~~ The establishment of current flow over the cathode area follows by outward spreading from this conducting plasma by diffusion.
- There are three phases of turn-on shown in fig. below.

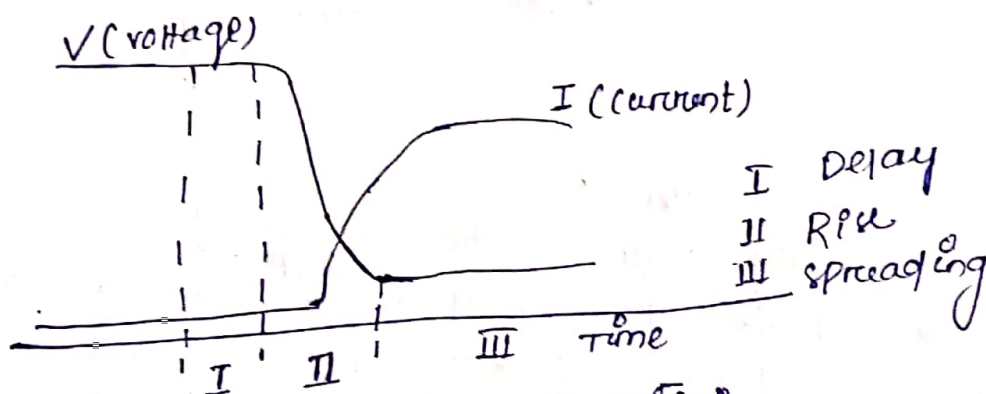


(Fig. Turn on characteristics)

- The delay time is associated with the establishment of regenerative action in response to the gate current.
- Regeneration is well established during the rise time.
- The current continues to increase during the spread time.

Turn-off :-


- All the three junctions are forward biased during on state and the base region contains excess minority & majority charge.
- This charge must either be swept out by an electric field or decay through regenerative processes within the silicon.
- The ckt voltage is reversed, the current falls to zero at a certain rate. Once the current reaches zero, the flow at the junctions can support this current by diffusion without building up of depletion layer.
- Peak value of reverse current is reached when excess hole concentration at the anode junction fallen to zero.
- At this time, thyristor is reverse voltage with depletion layer & the current decays as a result of charge recombination within the n-base region.
- The current is depend on the mean life time of carriers in n base region.
- The Turn-off process is show in figure below.

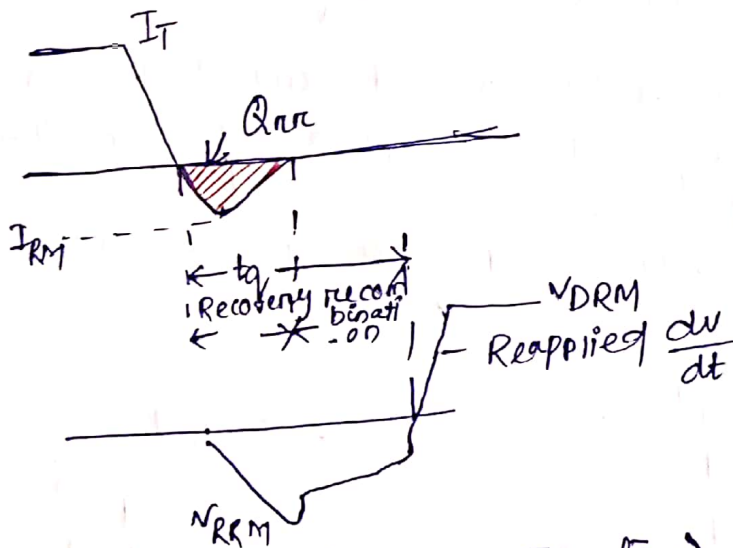

(Fig. Turn off characteristics)

- After current zero, thyristor doesn't ~~support~~ forward voltage. It acquires forward blocking capability but it with stand forward dv/dt .
- off state dv/dt attain only millisecond on has elapsed from ~~seconds~~.


Fig. below shows the current and voltage waveforms for a recovery and spontaneous turn on for a fixed dv/dt transient

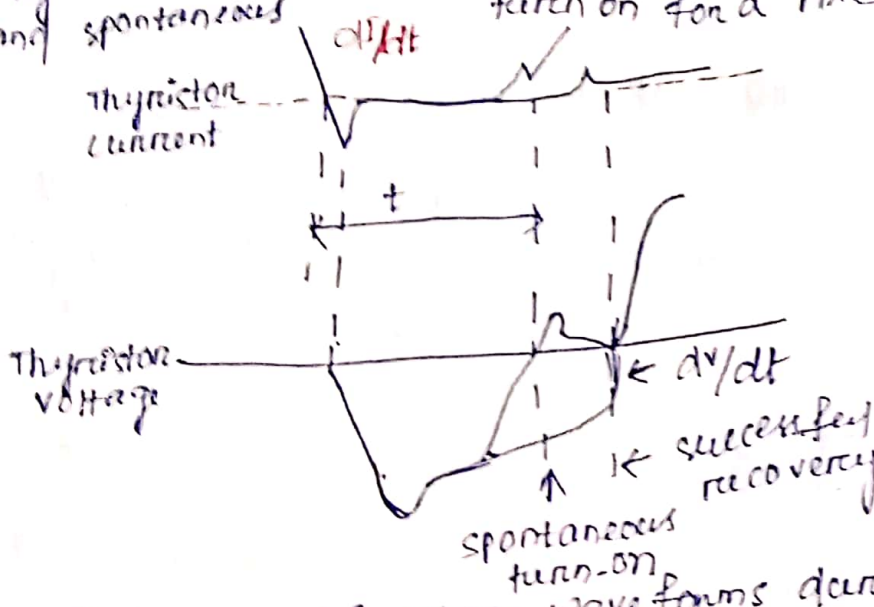

(Fig. current & voltage waveforms during the recovery)

Gate Drive :-

- A drive with rise time is to turn on the device with large di/dt .
- A single short pulse is to turn on the device, it does not have below holding current during conduction time.
- long pulses are to avoid blocking of the device.
- The gate $v-i$ characteristics are shown in figure below.
- Gate trigger is bounded by two lines A & B.
- The gate voltage and current having lower upper limits.
- The upper limits are fcn of the fund. temp.

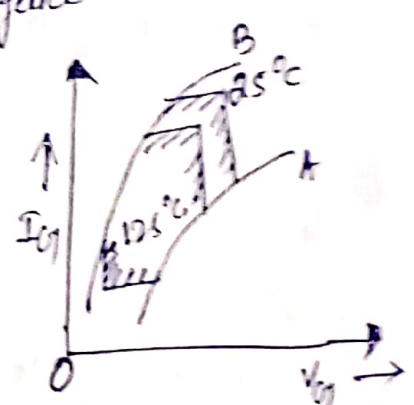

(Fig. gate characteristics)

- * Modern HVDC valve are fired from the optical signals.
- Those signals in turn are generated from the converter controller.
- The source is provided to each module by power supply unit.
- The gate pulses are generated in the gating and logic units in response to optical signals, transmitted via fiber-optic light guides separately to each module.
- The gating and thyristor status are monitored at the ground level from the signals sent through light guides (LED)

→ The diagram of typical module with one thyristor per Module is shown in below figure.

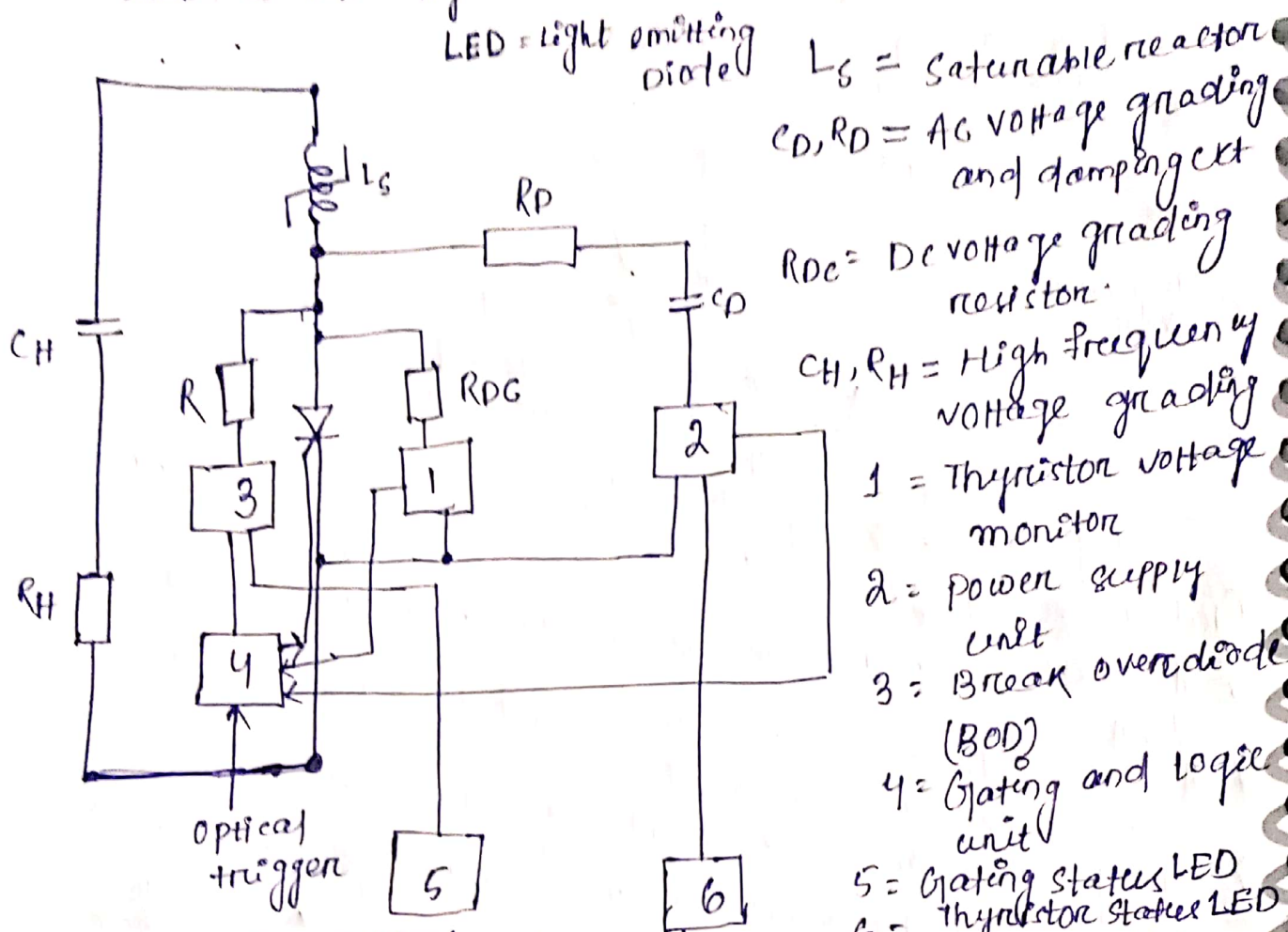


Fig. Typical valve Module (Source: Reference 22)


- The use of break over diode (BOD) is to sense overvoltage across the device & protect it by generating gate pulse.
- BOD firing, used for back-up when gating & logic unit fails.
- AC voltage grading is provided by resistor R_D & capacitor C_D in series.
- The resistor R_{DC} provides for DC voltage grading & it is also used for voltage measurement.
- The saturable reactor is used to protect the device against $\frac{di}{dt}$.
- C_H & R_H are used for high-frequency voltages as grading ext.

Thyristor Valve :- (L.V)

- A thyristor valve made up no. of devices are connected in series to provide voltage rating and connected in parallel to provide current rating.
- so modern devices does not need parallel connections.
- series connection of thyristor is for device ratings, transient over voltages & protection.
- valves placed indoors in a valve hall to protect against contamination and dust.
- valves are arranged in a single, double or quadruple configuration.
- valves are air insulated and cooled using air, water, oil or freon. so normally use is water.

Valve firing :-

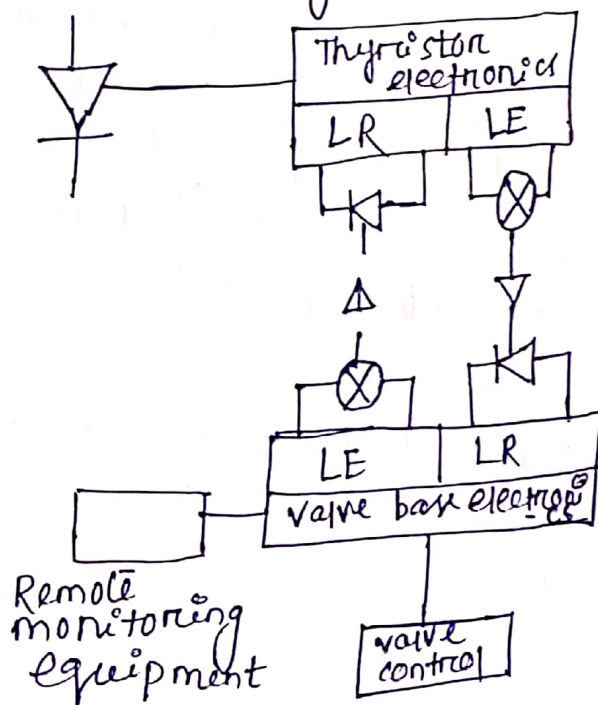- The basic valve firing scheme is shown in below figure.



LR - Light receiver
LE - Light emitter.

(Fig. valve firing scheme)

- The valve control generates firing signals.
- Each thyristor level receives the signal direct from separate fiber-cable.
- Each thyristor level is independent it only sharing duplicate light source at ground potential.
- Present day valve control unit is used return pulse system coupled with short pulses firing scheme.

- A light guide is send accurate pulse, when the voltage across the thyristor is enough and power unit is charged.
- at the time of firing pulses, demand it send to all thyristors control unit at a time.
- During normal operation, only one light pulses are generated in a cycle for each valve.
- Many light pulses are generated due to discontinuous current.


Valve design considerations:- (L.9)

- Design of valve must consider voltage and current stress during the normal & abnormal condⁿs.
- The voltage is excess it cause short ckt's on AC and DC systems.
- Due to dynamic overvoltage, it is crucial to determine the voltage ratings.
- The magnitude of dynamic voltage is depend on AC system strength.
- The ^{over}current cause the short ckt's across a converter bridge.
- The surge current ratings of a valve is limited both by transformer leakage and system impedance.
- The overload ratings of a valve is a funⁿ of the size of the device as well as ambient temp. and the cooling system.
- The losses in a valve include :-
 - The losses during on-state and switching losses.
 - Damper and grading ckt losses.
 - losses due to auxiliary power required for cooling.




- ~~probability~~ a generalised overvoltages and the design of valve component with damper ckt is facilitated by digital computer programmes which can be model the non-coherent turn on and turn off of the thyristor devices in a valve.

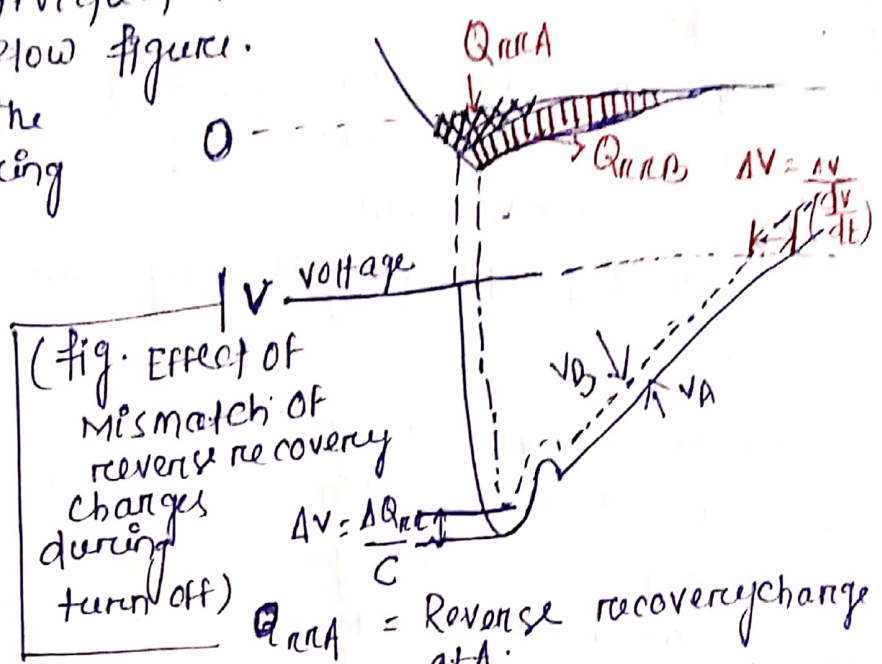- The non-coherent turn-on of a valve, voltage last level to be fired.
- The differences in the stored charges result in varying commutation margins in individual devices in an inverter valve & it is as shown in below figure.
- The below figure is the effect of charges during turn off.



(Fig. Effect of mismatch of reverse recovery charges during turn off)

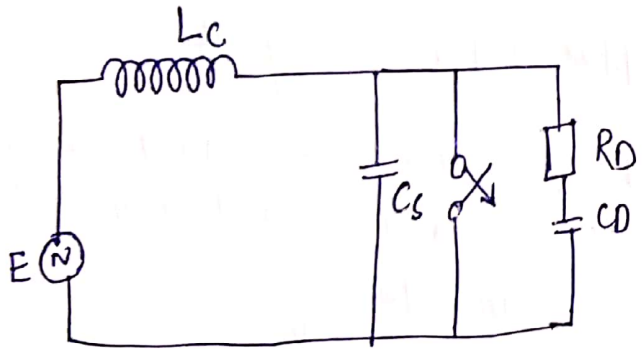- Q_{rrA} = Reverse recovery charge at A.
- Q_{rrB} = Reverse recovery charge at B.
- Q_{rr} = Reverse recovery charge
- C = stray capacitance




(Fig. simplified equivalent circuit during turn off)

- R_D =
- C_D =
- C_S = stray capacitance
- $L_S = L_s$ through source inductance

- The recovery voltage across the valve that has turned-off shows an overshoot that is due to the charging of the stray capacitance through the source inductance as shown in figure below.
- The reduction in short ckt Ratio (SCR) tends to reduce the max^m value of fault current in a valve.
- and not necessary to reduce stress, as the device failures occur due to over voltage.
- The low SCR can be give non sinusoidal voltage at converter bus which can cause commutation failures.
- The control of electrostatic and electromagnetic fields surrounding a valve is essential to avoid corona discharges and interference with sensitive electronic ccts.

→ The below figure shows the valve voltage waveform

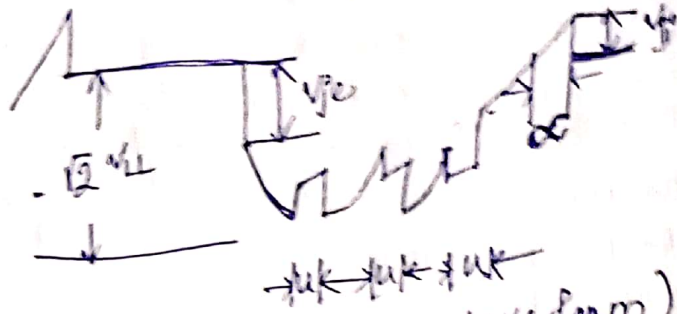→ The damper ckt is the significant component of overall losses.



→ The damper losses due to discontinuity in the valve voltage waveform.

→ 8 voltage jumps in a cycle. (fig. valve voltage waveform)

Suspended valve

→ Quadri-valve configuration is a compact valve hall & it is a tall in structures (upto 10 meter tall).

→ The suspension arrangement has spring and damper mechanism for mechanical isolation of the valve from the building vibrations.

→ The valve structure is flexible.

Water cooling

→ In place of air, water is replaced for cooling the valves from heat.

→ Water has several excellent qualities as a coolant:- high specific heat, high thermal conductivity, high heat transfer capability, low viscosity and low density.

→ It also electrolytic conductor.

→ In an HVDC valve, more than 95% of the heat losses are produced in thyristors, snubber ckt resistors & the valve reactors.

→ Water cooling is used to remove heat from components.

→ The cooling ckt needs to be optimized w.r.t


1. Thermal/hydraulic

2. Electrical performance.

→ conductivity of the water, the piping of the cooling ckt runs as a resistive n/w shunting thyristors, snubber etc.

→ A well cooling ckt configuration of a module, avoiding any flow of electrolytic current to metal parts.

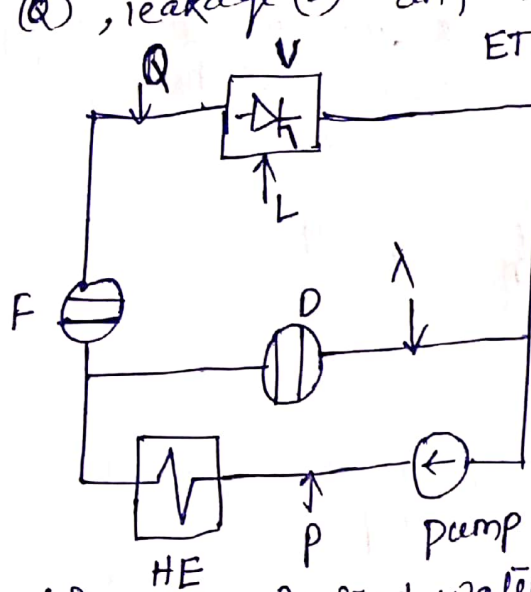- The basic configuration of the cooling ckt for a HVDC thyristor valve group is as shown in below figure.
- The quantities monitored are pressure (P), conductivity (λ), flow (Q), leakage (L) and water head (H).



- P - Pressure
- λ - conductivity
- Q - flow
- L - leakage
- H - water head
- ET - Expansion Tank
- V - valves
- D - Deionizer
- F - 50 μ Mechanical filter
- HE - Heat Exchanger

(Fig. De-ionized water circuit for cooling)

Valve Protection :- (L & Q)

- over voltage protection
- over temperature protection.

Over voltage protection :-

- A HVDC valve must be designed with (i) internal & (ii) external over voltages.
- The external sources for over voltage is (i) lightning & switching surges
- (ii) dynamic over voltages caused by load rejection.
- (iii) low order harmonic resonance in the AC system &
- (iv) injection of AC voltage on the DC line due to converter faults.
- valves can be protected by zinc oxide, gapless DC arresters from the over voltage.
- The over voltage in the forward dirⁿ can be controlled by protective firing of the thyristors in a valve.
- The over voltages in the fwd dirⁿ can also arise from partial recovery of a valve following turn-off process (in inverters).
- forward dv/dt protection is also required by sensing dv/dt measured across a level and turning on the device if the threshold is exceeded.

Over temperature protection :-

- The current ratings of a valve is determined by the ability of thyristors to withstand the recovery voltages following a worst case, credible fault current.

- This number is determined by j_{crit} , T_{lim} .
- An accurate prediction of j_{crit} , T_{lim} can be made, if pre-fault and post-fault current waveforms are specified.
- The thermal model of a thyristor is characterized by its transient thermal impedance R_{TH} & following is the eqn.

$$T(t) = \sum A_n h(t)$$

$$\text{where } T \text{ is the temp. rise.}$$

$$\frac{d\phi_n}{dt} + B_n \phi_n = B_n h(t)$$

where v_i
 A_n, B_n = parameters determined from tests.

v = on-state voltage drop

$$= v_0 (1 + \alpha T + \beta T^2) + r_0 (1 + \gamma T + \epsilon T^2) I + E_0 (273 + T)^{\epsilon} I$$

$$+ f_0 (1 + \gamma T + \delta T^2) \sqrt{I}$$

where $v_0, r_0, E_0, f_0, \alpha, \beta, \gamma, \epsilon, \delta$ and d are constants.
 when $h(t)$ is a unit step funⁿ.

$$T(t) = R_{TH}(t)$$


- when the j_{crit} , T_{lim} exceeds a critical level, the optical firing pulses to all the thyristors in a valve are inhibited.
- if two or more thyristors are connected in parallel, current sharing protection is provided to ensure that in case of a transient disturbance, one of the n thyristors does not extinguish.

Recent trends of HVDC valves :-


IGBT valve :- (L.V)

- BJT & MOSFET have complement each other.
- BJTs have lower conduction losses in the on state but longer switching times. ~~on the other~~
- MOSFETs can be turned on or off much faster, but their on state conduction losses are much longer.
- combine BJT and MOSFET monolithically in the same silicon wafer have led to the development of insulated gate Bipolar transistor (IGBT).

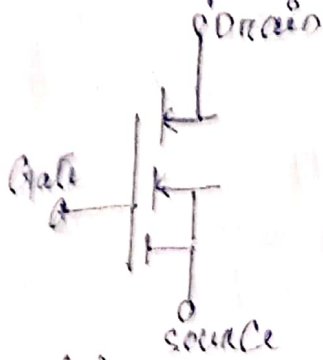→ The ckt symbols for IGBT are shown in fig. below.



(a)

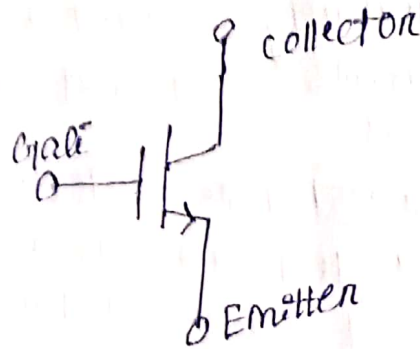

(b)

(fig. circuit symbols of IGBT)

→ IGBT combines a high impedance, low-power gate input with the power handling capacity of bipolar transistors.

→ And control is achieved by using a pattern of MOS transistor - ones.

→ The bipolar effect of the IGBT gives a self-limiting current.

→ The device is protected by turning it off within a few μ seconds.

→ IGBT is the linear control through the gate.

→ $\frac{di}{dt}$ and $\frac{dv}{dt}$ can be controlled during commutations.

→ IGBT valves are invariably used in VSC-HVDC converter stations.

→ To obtain rated current capability, the IGBT is made of a number of chips connected in parallel in the same housing.


→ The IGBT chip is designed to have only forward blocking capability, since the anti-parallel diode protects against voltage in the reverse dirⁿ. (free wheeling diode)

→ The IGBT is preferred choice for VSC based HVDC converters due to the following reasons:

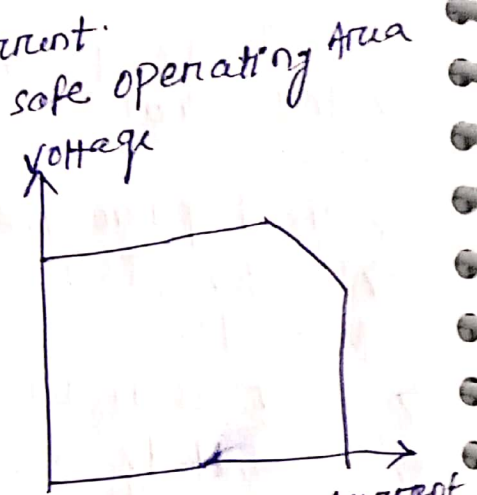1. It allows active voltage sharing.
2. Low power control which is advantageous at very high voltage levels.
3. transistor action that enables the converter to be turned off even in short ckt conditions.
4. High switching speeds, thus making high switching frequency feasible.

→ Valve design considerations:- (19)

- To ensure reliability, IGBT have few redundant devices to enable confirmed operation of the valve in case of failures.
- A faulty device cannot create an open ckt.
- A faulty device must enter into a short ckt mode and carry current until it is replaced during the scheduled maintenance period.
- Short ckt failure mode (SCFM) operation is very critical for series connected IGBT devices.
- IGBT is their capability to turn off current.
- This capability is defined in the switching safe operating area (SOA) as shown in below figure.
- Each valve may have two or more IGBT devices connected in series to provide the required voltage rating.
- Design an IGBT valve that maintains voltage sharing during switching & blocked states by gate control.
- power losses can be reduced by the selection of 3-level converters that operate at lower switching speeds.
- The design of cooling system for IGBT and FWD is similar to that of thyristor valves.
- The only difference is the increased losses in the IGBT valves.
- The losses in IGBT consists of on state conduction losses, and turn on and turn off loss.
- The losses in diode is negligible turn-on loss.
- As with thyristor valves, IGBT valves must be installed in specially designed valve halls or separate valve enclosures.



(Fig. Atypical SOA of IGBT)